

ECE412 Assignment 2

Han Yu
Feb 26, 2025

I. Reference Oscillator Phase Noise Model

The general phase noise equation is given by:

$$L(f) = \frac{h_3}{f^3} + \frac{h_2}{f^2} + \frac{h_1}{f} + h_0 \quad (1)$$

For the reference oscillator, since there is only $\frac{1}{f^2}$ dependence at low and middle frequency offsets, $h_3 = h_1 = 0$. Given that its phase noise has a noise floor of -160 dBc/Hz at large frequency offset, we get the relationship from (1): $L_{ref}(f) = -160 = 10\log_{10}(h_0)$, where we get $h_0 = 10^{-16} \frac{\text{rad}^2}{\text{Hz}}$. We are also told that at 10 kHz frequency offset the phase noise is -140 dBc/Hz, so we get $10^{-14} = \frac{h_2}{(10 \text{ kHz})^2} + 10^{-16} \approx \frac{h_2}{(10 \text{ kHz})^2}$, and $h_2 = 10^{-6} \frac{\text{rad}^2}{\text{Hz}}$. Overall, the phase noise equation is

$$L_{ref}(f) = \frac{10^{-6}}{f^2} + 10^{-16} \frac{\text{rad}^2}{\text{Hz}} \quad (2)$$

Fig.1 shows $L_{ref}(f)$ characteristics (in red) in dBc/Hz vs. frequency using a logarithmic frequency axis.

II. Voltage-Controlled Oscillator Phase Noise Model

The phase noise of the VCO can also be described by (1).

Given that there's no $\frac{1}{f^1}$ or $\frac{1}{f^2}$ dependence, we know that $h_1 = h_2 = 0$. Since a noise floor of -140 dBc/Hz appears at large f_m , we get the expression $L_{vco}(f) = -140 = 10\log_{10}(h_0)$, from which we then get $h_0 = 10^{-14} \text{rad}^2/\text{Hz}$. According to Table 1 in the assignment handout, at 1MHz offset frequency, the phase noise is -96 dBc/Hz, so $10^{-9.6} = \frac{h_3}{(1 \text{ MHz})^3} + 10^{-14} \approx \frac{h_3}{(1 \text{ MHz})^3}$, and we get $h_3 = 2.51 \times 10^8 \text{rad}^2/\text{Hz}$. Overall, the phase noise equation for this VCO is

$$L_{vco}(f) = \frac{10^{-2.51 \times 10^8}}{f^3} + \frac{10^{-14} \text{rad}^2}{\text{Hz}} \quad (3)$$

Fig.1 shows $L_{vco}(f)$ characteristics (in blue) in dBc/Hz vs. frequency using a logarithmic frequency axis.

III. Third-order PLL Design

Below are steps to design a third-order PLL. Design specifications are taken from the assignment handout and are summarized in Table 1.

Table 1. Third Order PLL Design Specifications

Surname start with	$f_{osc}(\text{GHz})$	$K_{vco}(\text{MHz}/\text{V})$	$L_{vco}@1\text{MHz}$	$f_{ref}(\text{MHz})$
Y	62-65	2200	-96 dBc/Hz	33.75

- We choose a single VCO frequency at 64.8 GHz within the given range, from which we can calculate $N = \frac{f_{osc}}{f_{ref}} = \frac{64.8 \text{ GHz}}{33.75 \text{ MHz}} = 1920$.
- VCO gain constant K_{osc} is 2200 MHz/V.
- Use $Q=0.5$ to achieve a relatively minimal peaking or fast settling of the loop.
- According to the *pll_bandwidth_choice_and_jitter.pdf*, a good choice for f_{3dB} is at the intersection point of $L_{vco}(f)$ and $L_{ref}(f) + 20\log_{10}(N)$. The $L_{ref}(f) + 20\log_{10}(N)$ characteristics can be found in Fig.1 (in green). This f_{3dB} point is selected specifically as it represents the frequency at which the contributions from the multiplied reference noise and the VCO noise are roughly equal. The intersection is roughly at $8.77 \times 10^5 \text{ Hz}$ as shown in Fig.1. Therefore, the loop bandwidth ω_{3dB} is $2\pi \times 8.77 \times 10^5 \text{ rad/s}$.
- For $Q=0.5$, $\omega_{pll} = 0.4\omega_{3dB} = 0.8\pi \times 8.77 \times 10^5 \text{ rad/s}$.
- For a charge-pump integer-N PLL, the following formula applies:

$$\frac{I_{ch}}{C_1} = \omega_{pll}^2 \frac{2\pi N}{K_{osc}} \quad (4)$$

We already know the values of ω_{pll} , N , and K_{osc} , (4) gives

$$\frac{I_{ch}}{C_1} = (0.8\pi \times 8.77 \times 10^5)^2 \times \frac{2\pi \times 1920}{2\pi \times 2200 \times 10^6} = 4.24 \times 10^6 \text{ V/s.}$$

Take $C_1 = 10 \text{ pF}$, then $I_{ch} = 42.5 \mu\text{A}$.

- Resistor R is chosen so that $\omega_z = Q\omega_{pll} = 0.5 \times 0.8\pi \times 8.77 \times 10^5 = 0.4\pi \times 8.77 \times 10^5 \text{ rad/s}$. Then, $R = \frac{1}{\omega_z C_1} = 226.8 \text{ k}\Omega$.
- Finally, the de-glitching capacitor $C_2 = \frac{C_1}{10} = 1 \text{ pF}$.

Table 2. below summarizes the design parameters of the 3rd order PLL.

Table 2. Summary of the Third Order PLL Design Parameters

$h_{2,ref}[\text{rad}^2/\text{Hz}]$	$h_{0,ref}[\text{rad}^2/\text{Hz}]$	$h_{3,vco}[\text{rad}^2/\text{Hz}]$	$h_{0,vco}[\text{rad}^2/\text{Hz}]$	
10^{-6}	10^{-16}	2.51×10^8	10^{-14}	
N	Q	$\omega_{3dB}[\text{rad/s}]$	$\omega_{pll}[\text{rad/s}]$	$\omega_z[\text{rad/s}]$
1920	0.5	$2\pi \times 8.77 \times 10^5$	$0.8\pi \times 8.77 \times 10^5$	$0.4\pi \times 8.77 \times 10^5$
$I_{ch}[\mu\text{A}]$	$R[\text{k}\Omega]$	$C_1[\text{pF}]$	$C_2[\text{pF}]$	
42.5	226.8	10	1	

The open-loop response of PLL is defined as:

$$L(s) = \frac{K_{pd}K_{lp}K_{osc}H_{lp}(s)}{Ns} \quad (5)$$

For a 3rd-order (Type-II) PLL, the loop filter gain is:

$$K_{lp}H_{lp}(s) = \frac{1}{s(C_1 + C_2)} \cdot \frac{1 + sRC_1}{1 + sR\left(\frac{C_1C_2}{C_1 + C_2}\right)} \quad (6)$$

We also know that $K_{pd} = \frac{I_{ch}}{2\pi}$. Substituting the design parameters into (5), we get:

$$L(s) = \frac{I_{ch}K_{osc}}{2\pi \cdot N} \cdot \frac{1 + sRC_1}{s^2(C_1 + C_2) \left(1 + sR\left(\frac{C_1C_2}{C_1 + C_2}\right)\right)} \quad (7)$$

The bode plots of the PLL loop gain (i.e., $L(s)$) is shown in Fig.2. The unity gain frequency ω_t is found when the magnitude response is at 0dB, which gives roughly $\omega_t = 1.46 \text{ MHz}$. At ω_t , the phase response increases from -180° to -124° , which indicates a phase margin of 56° . Fig.3 shows the magnitude response of the jitter transfer function, where we found $\omega_{3dB} = 1.49 \text{ MHz}$. The $L_{out}(f)$ characteristics (in yellow) is plotted in Fig.1. At 1 MHz offset frequency, the main phase noise contributor is the VCO since $L_{out}(f_m = 1 \text{ MHz})$ is the same as $L_{vco}(f_m = 1 \text{ MHz})$.

The rms random jitter can be calculated using the formula:

$$\sigma_{jrms} = \frac{1}{2\pi f_{out}} \cdot \theta_{rms} \quad (8)$$

, where

$$\theta_{rms} = \sqrt{2 \int_0^\infty L(f_m) df_m} \quad (9)$$

is the rms phase error.

To calculate the rms phase error, we need to know the contribution of noise sources. At low frequency, i.e. frequencies below 10^5 Hz , L_{ref} dominates, especially the term $\frac{10^{-6}}{f^2}$. Between 10^5 Hz and the loop bandwidth, $8.77 \times 10^5 \text{ Hz}$, the 10^{-16} term from L_{ref} is the dominant noise source. At frequencies above the loop bandwidth, VCO becomes the main source of phase noise: Between $8.77 \times 10^5 \text{ Hz}$ and $3 \times 10^7 \text{ Hz}$, the $\frac{10^{-2.51 \times 10^8}}{f^3}$ term from L_{vco} is the main noise source. Finally, between $3 \times 10^7 \text{ Hz}$ and 10^{10} Hz , the 10^{-14} term from L_{vco} dominates.

Integrate all the noise contributions above and we get the rms phase error from (9):

$$\begin{aligned} \theta_{rms} &= \left(2 \left[\int_{10^3}^{10^5} \frac{10^{-6}}{f^2} df_m + \int_{10^5}^{8.77 \times 10^5} 10^{-16} df_m + \int_{8.77 \times 10^5}^{3 \times 10^7} \frac{10^{-2.51 \times 10^8}}{f^3} df_m \right. \right. \\ &\quad \left. \left. + \int_{3 \times 10^7}^{10^8} 10^{-14} df_m \right] \right)^{\frac{1}{2}} = 1.81 \times 10^{-2} \text{ rad} \end{aligned}$$

Now, substitute θ_{rms} into (8) to calculate the rms PLL jitter:

$$\sigma_{jrms} = \frac{1}{2\pi f_{out}} \cdot \theta_{rms} = \frac{1}{2\pi \times 64.8 \text{ GHz}} \cdot 1.81 \times 10^{-2} = 0.044 \text{ ps}.$$

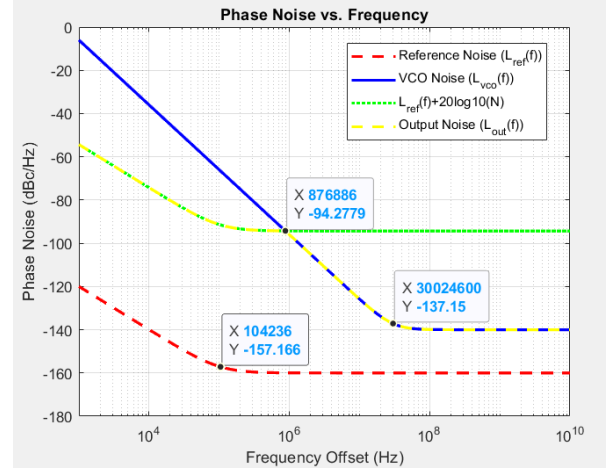


Fig.1 Phase Noise vs. Frequency for $L_{ref}(f)$, $L_{vco}(f)$, $L_{ref}(f) \times N^2$ and $L_{out}(f)$. 3dB bandwidth is at the intersection of $L_{vco}(f)$ (in blue) and $L_{ref}(f) \times N^2$ (in green).

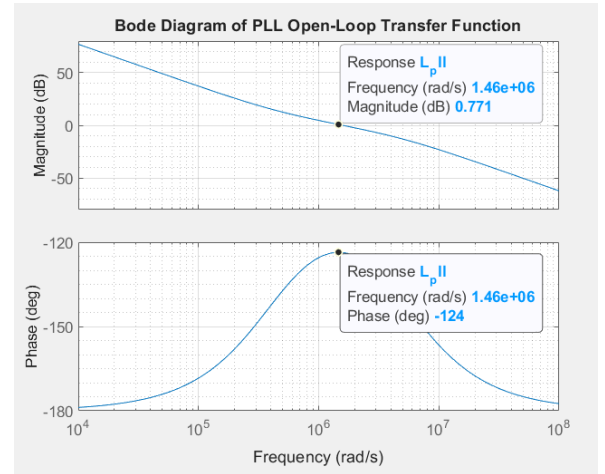


Fig.2 Magnitude (in dB) and phase response of the PLL loop gain in the phase domain. The unity gain frequency (ω_t) is marked in the plots.

 


Fig.3 3dB bandwidth of the PLL jitter transfer function